


# ELECTRICAL SCIENCE-II

## (15B11EC211)

### **UNIT 1**

### **LECTURE 2**

# Example1

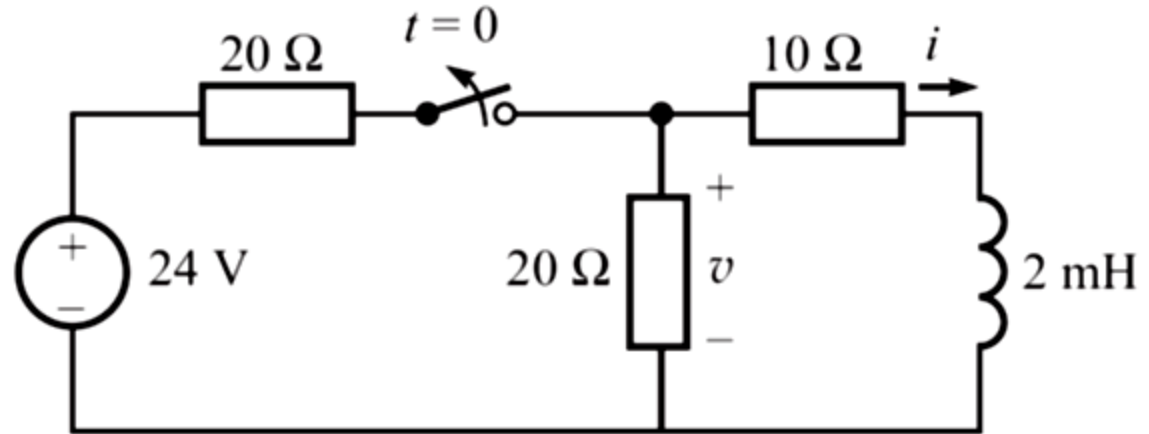

The circuit has been in the condition shown for a long time. The switch is opened at  $t = 0$ .

- (i) Determine the current  $i(0+) = I_0$ .
- (ii) Find  $v_R$  across 20-Ω resistor at the instant just after the switch is opened.
- (iii) Find  $v_L$  across the inductor immediately after the switch is opened.

**Solution :** (i) Under steady-state condition, the voltage drop across an inductor is zero and it behaves as a short-circuit. The equivalent resistance faced by the 24-V source is

$$R_{eq} = 20\Omega + (20\Omega \parallel 10\Omega) = 26.67\Omega$$

The current supplied by the 24-V source,


$$I = \frac{V}{R_{eq}} = \frac{24}{26.67} = 0.9 \text{ A}$$

By current division,

$$I_L = 0.9 \times \frac{20}{20+10} = 0.6 \text{ A}$$

Immediately after the switch is opened, the current through the inductor remains the same. Hence,
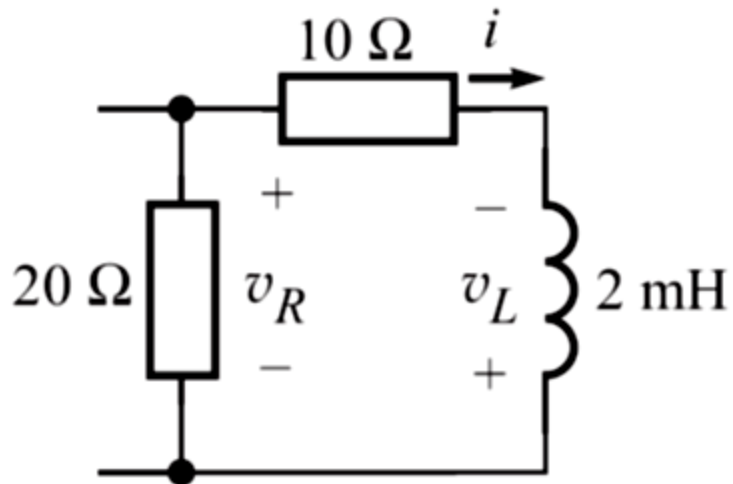
$$i(0^+) = I_0 = \mathbf{0.6 \text{ A}}$$



The circuit after the switch is opened ( $t > 0$ ).


(*ii*) The voltage across the  $20\text{-}\Omega$  resistor,

$$v_R = (-I_0)R = -0.6 \times 20 = \mathbf{-12 \text{ V}}$$


(iii)

$$e = L \left. \frac{di}{dt} \right|_{t=0} = L \times \left( I_0 \times \frac{R}{L} \right) = I_0 R = 0.6 \times (20 + 10) = \mathbf{18 \text{ V}}$$
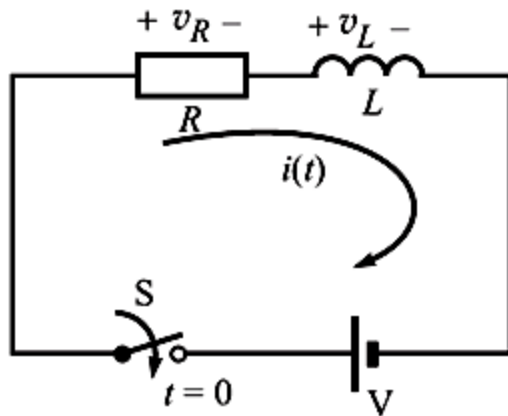
# Growth of Current in Series *RL* Circuit



(a) The circuit.

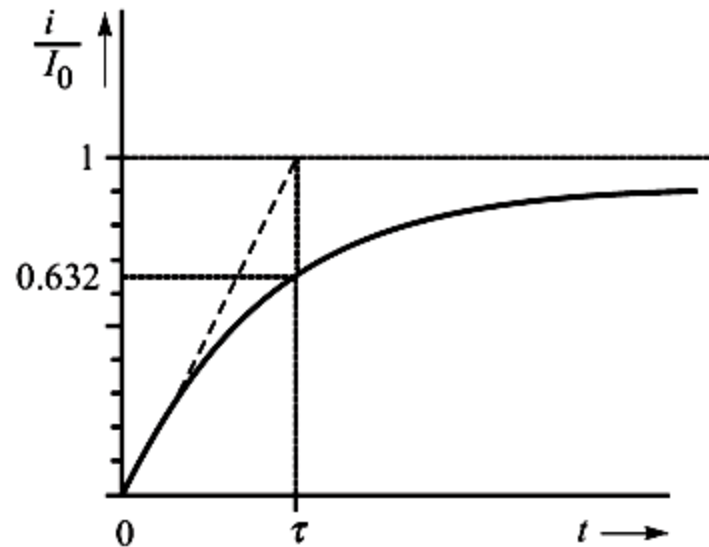

(b) The response.

- Since the current in an inductor cannot change by a finite amount in zero time, we must have  $i(0+) = 0$ .
- After  $t = 0$ , the current slowly increases and approaches its steady state value  $I_0 = V/R$ .

The response to this circuit for  $t > 0$  can be found as

$$i(t) = I_0(1 - e^{-t/\tau})$$

The value of  $i(t)/I_0$  at  $t = \tau$ ,

$$\frac{i(\tau)}{I_0} = (1 - e^{-1}) = (1 - 0.368)$$

or  $i(\tau) = 0.632I_0$

- Thus, in one time constant the response rises to 63.2 % of its final value.
- It takes about five time constants for the current to grow to its final steady state value.

# Rate of Growth of Current

The initial rate of growth of current is given by the slope of the curve at the origin.

$$\left. \frac{di}{dt} \right|_{t=0} = - \left( - \frac{I_0}{\tau} \right) e^{-t/\tau} \Big|_{t=0} = \frac{I_0}{\tau} = \frac{V}{R} \frac{R}{L} = \frac{V}{L}$$

- Thus, the smaller the value of  $L$ , the faster the current rises to its final value.



## Example 2

A coil having an inductance of 14 H and a resistance of  $10\ \Omega$  is connected to a dc voltage source of 140 V, through a switch.

- (a) Calculate the value of current in the circuit at an instant 0.4 s after the switch has been closed.
- (b) Once the current reaches its final steady state value, how much time it would take the current to drop to 8 A after the switch is opened ?

## Solution :

The time constant,  $\tau = L / R = 14 / 10 = 1.4 \text{ s}$

(a) The final steady state value of the current,

$$I_0 = \frac{V}{R} = \frac{140}{10} = 14 \text{ A}$$

The value of current at  $t = 0.4 \text{ s}$  is given by


$$i = I_0(1 - e^{-t/\tau}) = 14(1 - e^{-0.4/1.4}) = \mathbf{3.479 \text{ A}}$$

(b) For decaying current,


$$i(t) = I_0 e^{-t/\tau} \quad \text{or} \quad 8 = 14e^{-t/1.4} \quad \text{or} \quad e^{-t/1.4} = 0.5714$$

$$-\frac{t}{1.4} = \ln 0.5714 = -0.5596 \quad \Rightarrow \quad t = \mathbf{0.7834 \text{ s}}$$
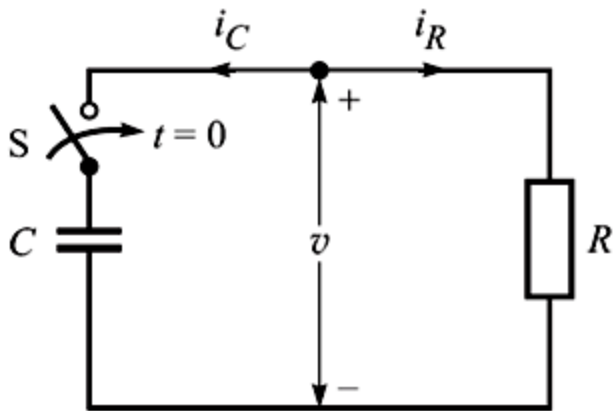
# The Simple $RC$ Circuit (Discharging of a Capacitor)



(a) The circuit.

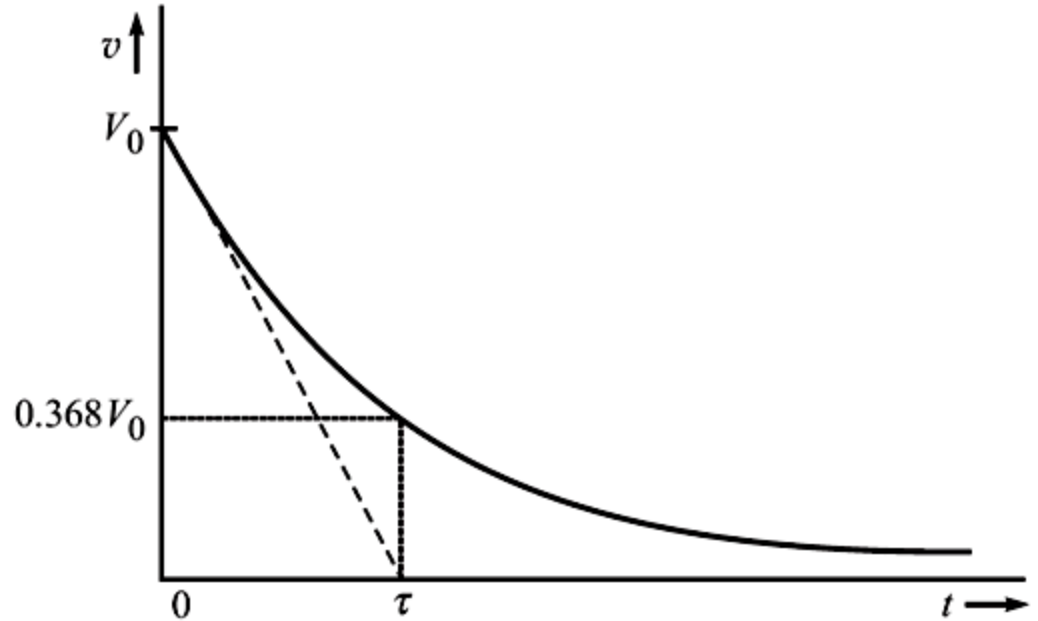

(b) The voltage response.

The total current leaving the node at the top of the circuit diagram must be zero. Therefore,

$$i_C + i_R = 0 \quad \text{or} \quad C \frac{dv}{dt} + \frac{v}{R} = 0 \quad \text{or} \quad \frac{dv}{dt} + \frac{v}{CR} = 0$$



The solution of this equation is

$$v = V_0 e^{-t/RC} = V_0 e^{-t/\tau}$$

The time constant,  $\tau = RC$

As per definition of the time constant  $\tau$ , the slope of the curve at  $t = 0$  is given as  $-V_0/\tau$ .

# Charging of a Capacitor

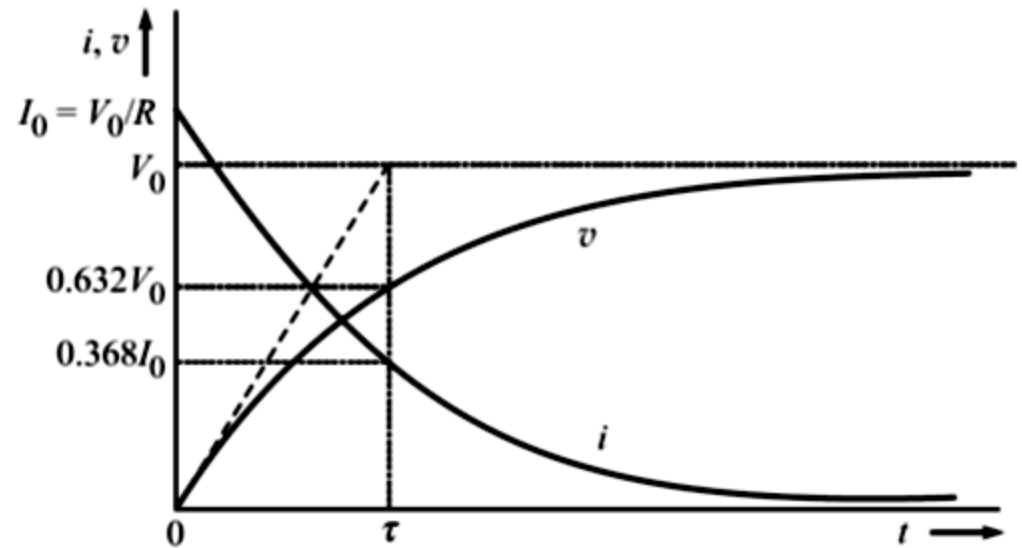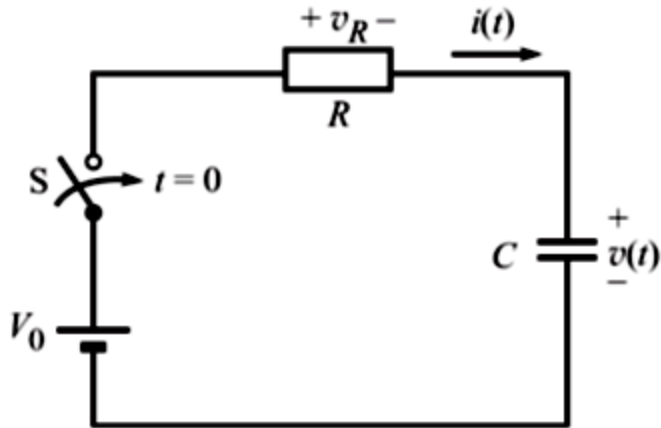

(a) The circuit. (b) The voltage and current response.

- Since the voltage across a capacitor cannot change instantaneously, we must have  $v(0^+) = v(0^-) = 0$
- It means that initially the capacitor behaves as a short-circuit. The value of the initial current in the circuit,

$$i(0^+) = I_0 = \frac{V_0}{R}$$

$$v(t \rightarrow \infty) = V_0 \quad \text{and} \quad i(t \rightarrow \infty) = 0$$

The response of the circuit can be determined as

$$v = V_0 (1 - e^{-t/\tau})$$

# References

1. R.C.Dorf and James A. Svoboda, "Introduction to Electric Circuits", 9th ed, John Wiley & Sons, 2013.
2. Charles K. Alexander, Matthew N.O. Sadiku, "Fundamentals of Electric Circuits", 6th Edition, Tata McGrawHill, 2019.