

ES-II (Assignment-2)

Q.1. $f = \frac{1}{\tau} = \frac{1}{q n A h} = \frac{1}{1.6 \times 10^{-19} \times 10^{17} \times 800}$

$= 0.078 = 0.08 \text{ cm}.$

Q.2. Clipper Circuits are the Circuits that clip off or removes a portion of an input signal, without causing any distortion to the remaining part of the wave form.

Clippers are basically wave-shaping Circuits that control the shape of an output waveform.

Clippers circuit are basically termed as protection devices.

Classification of Clipper Circuit

→ Positive Clipper Circuit

→ Negative Clipper Circuit

The Clipper circuit that is intended to attenuate positive portions of the input signal can be termed as a positive clipper.

We have following types :

- Positive Series Clipper :-
 - positive series clipper with positive V_r (Reference Voltage)
 - positive series clipper with negative V_r
- Positive Shunt Clipper :-
 - positive shunt clipper with positive V_r
 - positive shunt clipper with negative V_r

The clipper circuit that is intended to attenuate negative portions of the input signal can be termed as negative clipper.

- Negative series clipper :-
 - Negative series clipper with positive V_r
 - Negative series clipper with negative V_r
- Negative shunt clipper :-
 - Negative shunt clipper with positive V_r
 - Negative shunt clipper with negative V_r

Clamper Circuit :

A Clamper circuit can be defined as the circuit that consists of a diode, a resistor & a capacitor that shifts the waveforms to a desired DC level without changing the actual appearance of the applied signal.

In a clamper circuit, a vertical shift of upward or downward takes place in the output waveform.

There are few types of Clamper circuit -

- positive clamper
 - positive clamper with positive V_r
 - positive clamper with negative V_r
- Negative clamper
 - Negative clamper with positive V_r
 - Negative clamper with negative V_r

Q.3. The configuration in which the emitter is connected between the collector & base is known as a common emitter configuration (CE).

→ Input characteristic : The variation of emitter current (I_E) with Base-emitter voltage (V_{BE}) keeping collector-emitter voltage (V_{CE}) constant.

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_E} \quad \left| \quad V_{CE} = \text{constant} \right.$$

→ Output characteristics : The variation of collector current (I_C) with collector-emitter voltage (V_{CE}) keeping the base current (I_B) constant.

$$R_{out} = \frac{\Delta V_{CE}}{\Delta I_C} \quad | \quad I_B = \text{constant}$$

In CB Configuration, the Base terminal of the transistor will be connected common between the output and the input terminals (CB)

→ Input characteristics : The Variation of emitter current (I_E) with Base-emitter voltage (V_{BE}), keeping collector base voltage (V_{CB}) constant.

$$R_{in} = \frac{\Delta V_{BE}}{\Delta I_E} \quad | \quad V_{CB} = \text{constant}$$

→ Output characteristics : The variation of collector current (I_C) with collector-base voltage (V_{CB}). Keeping the emitter current (I_E) constant.


$$R_{out} = \frac{\Delta V_{CB}}{\Delta I_C} \quad | \quad I_E = \text{constant}$$

In CE Configuration, the collector terminal of the transistor will be connected common between the output & the input terminal.

→ Input characteristics : The Variation of emitter current (I_E) with collector-base voltage (V_{CB}), keeping collector base voltage (V_{CE}) constant.

→ Output characteristics : The Variation of emitter current (I_E) with collector-emitter voltage (V_{CE}), keeping the base current (I_B) constant.

Q.4.

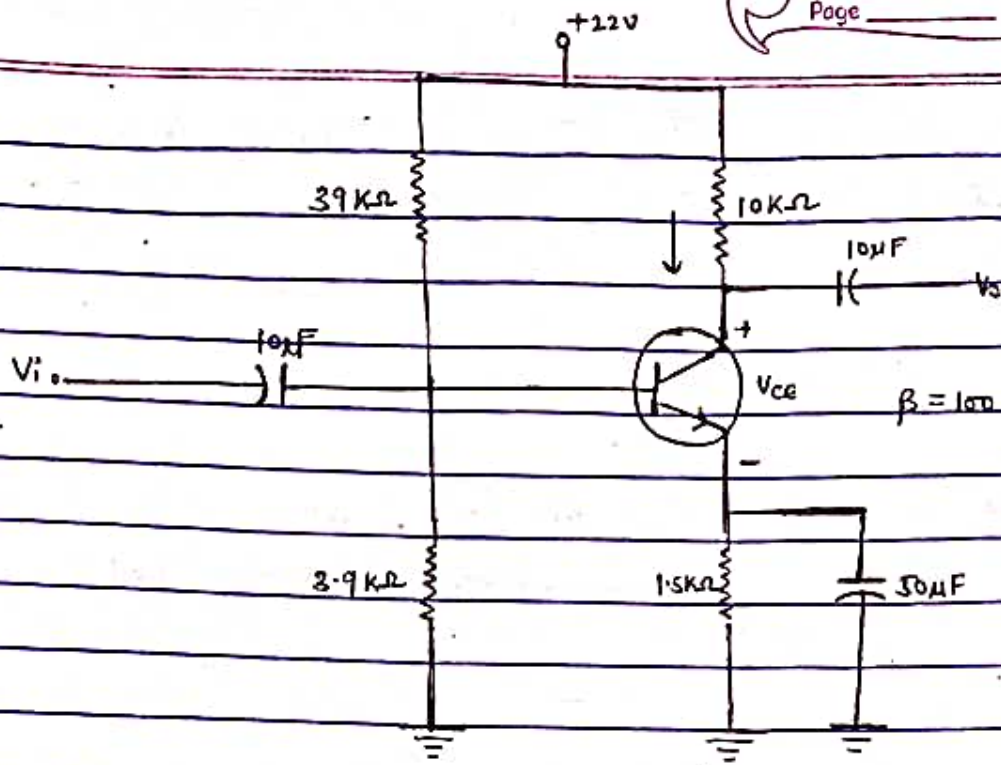

$$R_{th} = R_1 \parallel R_2 = \frac{(39k\Omega)(3.9k\Omega)}{(39k\Omega + 3.9k\Omega)} = 3.55k\Omega$$

$$E_{th} = \frac{R_2 V_{cc}}{R_1 + R_2} = \frac{(3.9k\Omega) 22V}{39k\Omega + 3.9k\Omega} = 2V$$

$$I_B = \frac{E_{th} - V_{be}}{R_{th} + (\beta + 1)R_E} = \frac{2 - 0.7V}{3.55 + 101 \times 1.5}$$

$$= \frac{1.3}{3.55 + 151.5} = 8.38 \mu A$$

$$I_C = 100 \times 8.38 = 0.838 mA$$

$$V_{ce} = V_{cc} - I_C (R_C + R_E) = 22 - (0.838)(10 + 1.5)$$

$$= 22 - 9.63 = 12.37V \checkmark$$